

Homework 7

Andrei Tumbar

02-24-2021

Problem 9

Create a circuit that outputs 1 if four consecutive inputs are equal.

 


Figure 1: Circuit which compares two numbers and outputs a 1 if they are equal for four consecutive clocks.

The comparison is done via a XNOR gate which will output a 1 if the two inputs are equal. The previous 3 comparisons will be held in the D-flip-flop. All of the previous comparisons as well as the current comparison must be true in order to produce a high output.

Problem 10

(See VHDL file)

Exercise 22

This FSM will output a 1 if the sequence AB is seen in the input. It will always output 0 otherwise.

Table 1: State-transistion and output table

Input	State	Next State	Output
A	00	01	0
\bar{A}	00	00	0
B	01	10	0
\bar{B}	01	00	0
	10	00	1

AB	Q_1Q_0			
	00	01	11	10
00	0	0	0	0
01	0	1	0	0
11	0	1	0	0
10	0	0	0	0

(a) K-map for Q_1'

AB	Q_1Q_0			
	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	0	0	0
10	1	0	0	0

(b) K-map for Q_0'

Figure 2: K-Map for Exercise-22 state machine

$$\begin{aligned}
 Y &= Q_1 \bar{Q}_0 \\
 Q_1' &= \bar{Q}_1 Q_0 B \\
 Q_0' &= \bar{Q}_0 \bar{Q}_0 A
 \end{aligned}$$