

## Lab 4 prelab

Andrei Tumbar

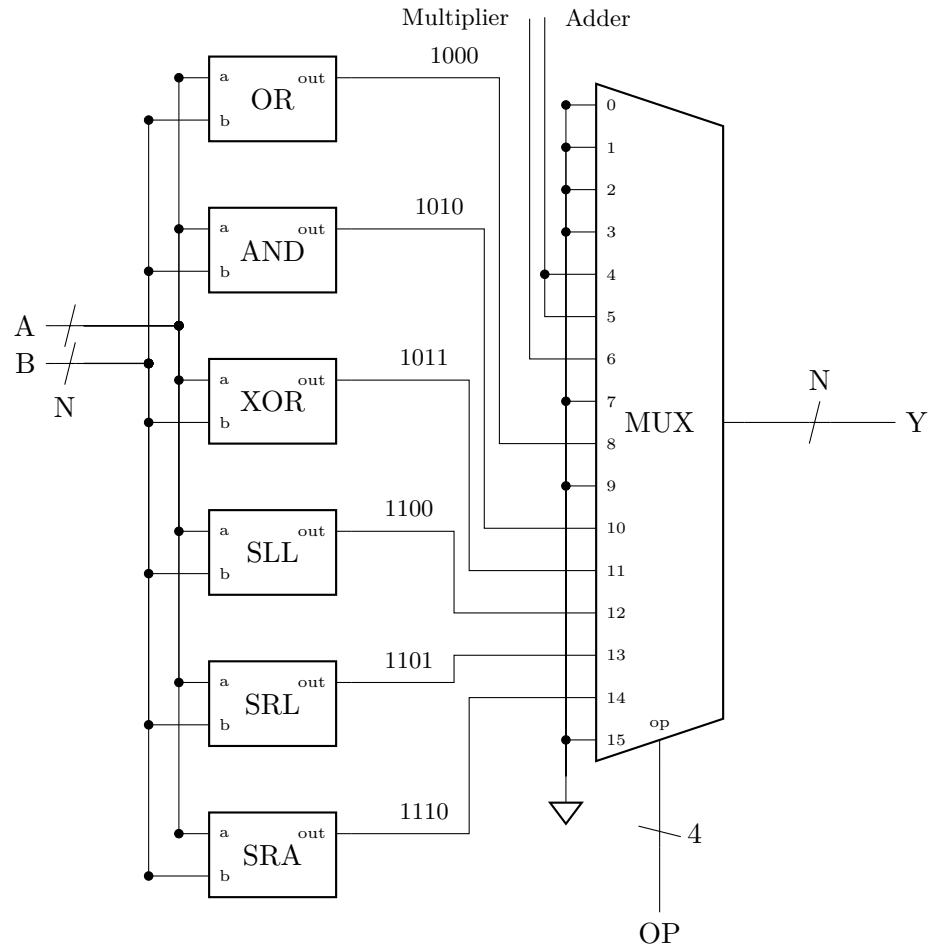


Figure 1: Layout of the N-bit ALU with eight operations

This ALU will expand on the ALU create in Exercise 1. It will support three more operations: multiply, add, subtract. The addition and subtraction come from the same circuit.

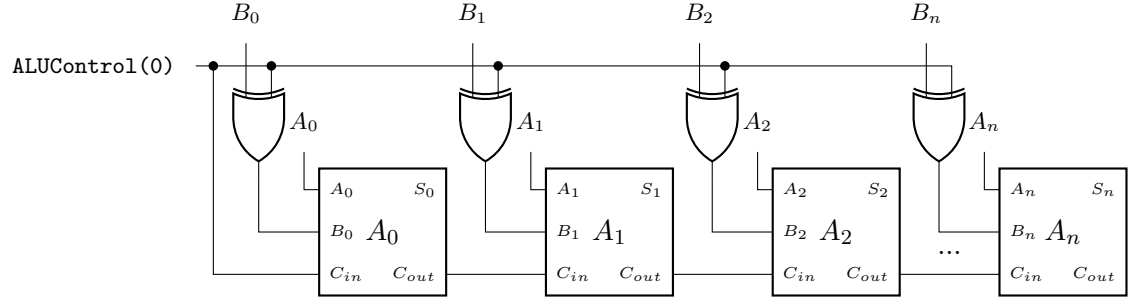


Figure 2: N-bit ripple-carry adder/subtractor.

The output of the adder/subtractor can be found in  $S_n$  ports on each full adder. A set LSB on  $ALUControl$  will select subtraction and compute  $A-B$ .

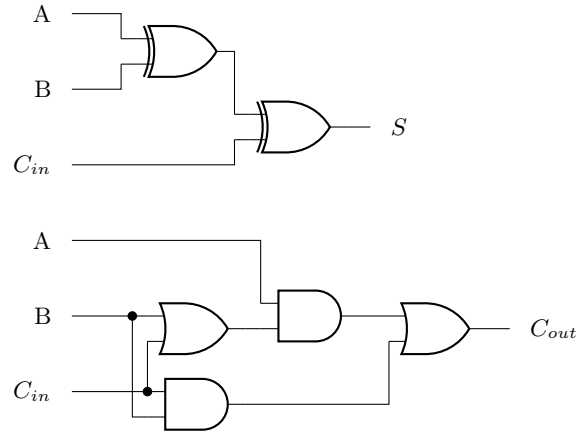


Figure 3: Full-adder circuit diagram

Figure 3 shows the inner circuit diagram of the full adders used in the ripple-carry adders (Figure 2) and the multiplier.

To multiply numbers  $A$  and  $B$ , a circuit diagram using a grid of full adders is shown.  $A$  and  $B$  are each  $N/2$  bits long and the resultant product is  $N$  bits long.

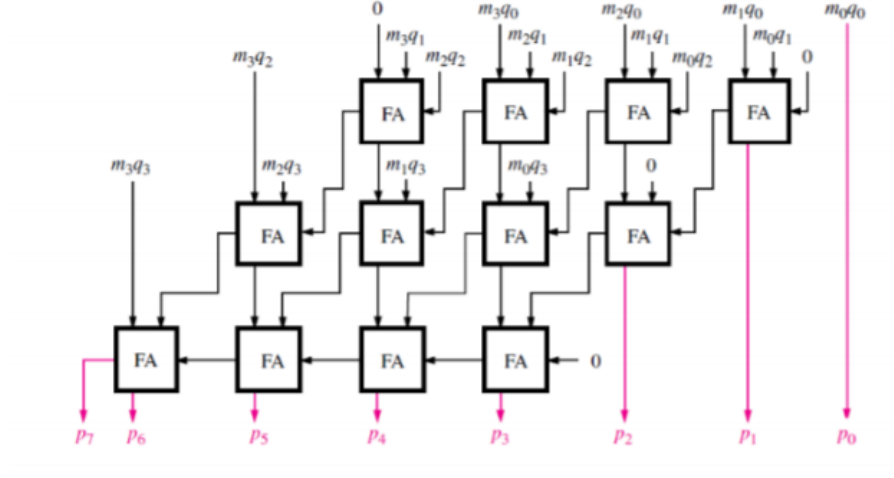


Figure 4: Diagram of a 4-bit unsigned integer multiplier circuit